```
clear all
close all
syms R C Ep t w
netlist={'V1 1 0 Ep'
    'R1 1 2 R'
    'R2 2 4 R'
    'C1 2 0 2*C'
    'C2 1 3 C'
    'C3 3 4 C'
    'R3 3 0 R/2'};
[X name]=fspice(netlist)
```

** fspice 2.43 ** (c) Frederic Martinez X =

$$\begin{pmatrix}
Ep \\
\underline{Ep (C R s + 1)} \\
\sigma_{1}
\end{pmatrix}$$

$$\frac{C Ep R s (C R s + 1)}{\sigma_{1}}$$

$$\underline{Ep (C^{2} R^{2} s^{2} + 1)} \\
\sigma_{1}$$

$$-\frac{4 Ep (R C^{2} s^{2} + C s)}{\sigma_{1}}$$

where

$$\begin{split} \sigma_1 &= C^2\,R^2\,s^2 + 4\,C\,R\,s + 1 \\ \text{name = 1} \times 5 \text{ cell} \\ \text{'V(1)'} & \text{'V(2)'} & \text{'V(3)'} & \text{'V(4)'} \\ \end{split}$$

```
H=X(4)/X(1); %TL de la tension au noeud 4 sur TL de la tension au noeud 1
f=20; % en Hz, à faire varier 20, 170 puis 10000 Hz
e=cos(2*pi*f*t)*heaviside(t); %e(t)
E=laplace(e) %TL de e(t)
```

E =

$$\frac{s}{s^2 + 1600 \,\pi^2}$$

```
S=E*H; % TL de s(t)
st=ilaplace(S) %TL inverse de S
```

st =

$$\frac{2560000\,\pi^{4}\,\sigma_{2}\,C^{4}\,R^{4}-256000\,\pi^{3}\,\sigma_{4}\,C^{3}\,R^{3}-3200\,\pi^{2}\,\sigma_{2}\,C^{2}\,R^{2}+160\,\pi\,\,\sigma_{4}\,C\,\,R+\sigma_{2}}{\sigma_{1}}+\frac{25600\,C^{2}\,R^{2}\,\pi^{2}\,\mathrm{e}^{-\frac{2\,t}{C\,R}}}{2}$$

where


```
\sigma_1 = 2560000 \,\pi^4 \,C^4 \,R^4 + 22400 \,\pi^2 \,C^2 \,R^2 + 1
```

$$\sigma_2 = \cos(40 \,\pi \,t)$$

$$\sigma_3 = \frac{\sqrt{3} t}{C R}$$


$$\sigma_4 = \sin(40 \pi t)$$
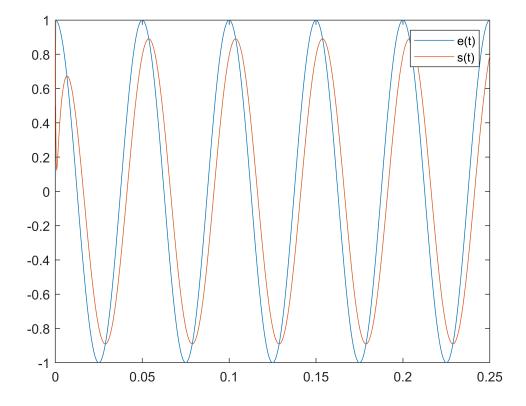
```
t=linspace(0, 5/f,1000); R=1e3; C=1e-6;
enum=subs(e);
snum=subs(st);
plot(t,enum, t,snum)
legend('e(t)','s(t)')
```



```
s=1j*w;
H=subs(H);
w=logspace(0,6,1000);
```
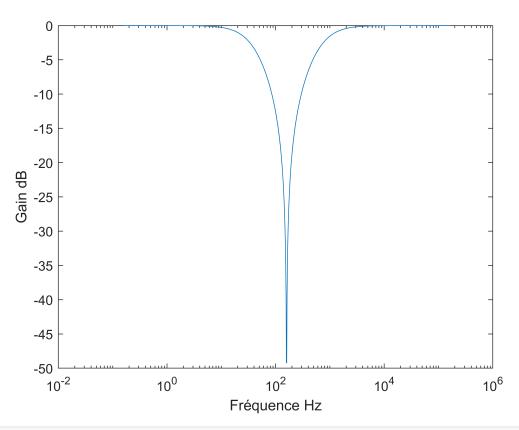
```
H=subs(H);
figure
semilogx(w/(2*pi),20*log10(abs(H)))
xlabel('Fréquence Hz')
ylabel('Gain dB')
```



```
figure
semilogx(w/(2*pi), angle(H)*180/pi)
xlabel('Fréquence Hz')
ylabel('Phase en degré')
```

